
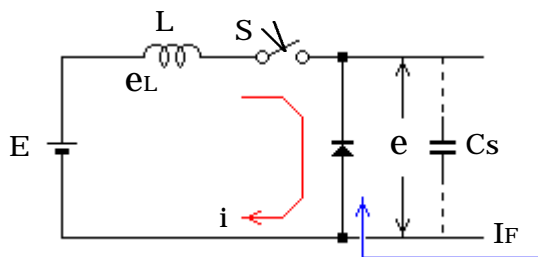


Hitachi Power Devices Technical Information PD Room

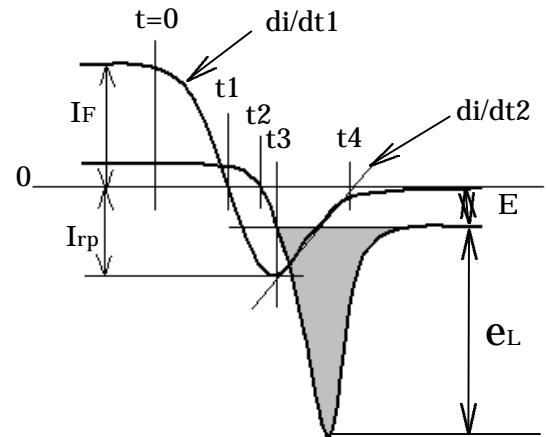This month, we will describe how overvoltage occurs due to the hole accumulation effect of a diode device. This phenomenon takes place when a diode shifts from an on state to an off state by circuit operation (when in commutation). How this occurs is described using a circuit indicated below and a waveform that occurs when in commutation.



Equivalent circuit when in commutation



How overvoltage occurs

- 1) I_F flows first in the forward direction of the diode.
- 2) Commutation starts at $t = 0$.
- 3) At this time, if the diode's forward voltage drop is ignored, the current declines at E/L , because $E = L \frac{di}{dt1}$. ----- (1)
- 4) At t_1 and later, a reverse recovery current flows due to the carrier accumulation effect of the diode.
- 5) At the point t_2 , the junction is restored and the diode starts restoring its bulk.
- 6) At t_3 , the reverse recovery current reaches its maximum, and the voltage applied to the diode becomes source voltage E .

$$I_{rp} = \text{maximum} \quad \therefore \frac{di}{dt1} = 0 \quad \therefore L \frac{di}{dt1} = 0 \quad \therefore e = E$$

- 7) At t_3 and later, the reverse recovery current attenuates due to the disappearance of carriers in the diode bulk. At this time, the diode is subjected to a commutation surge voltage of

$$e = E + e_L = E + L \frac{di}{dt2} \text{ -----(2)}$$


Calculating overvoltage

If the diode bulk recovery occurs quickly (that is, if the lag between t_3 and t_4 is short), L 's energy $\frac{1}{2} L I_{rp}^2$ changes quickly, so that an overvoltage of

$L \frac{di}{dt2}$ occurs. In the calculation model

in the right-hand figure, let $C_s = C_j + C_s'$. ----- (3)

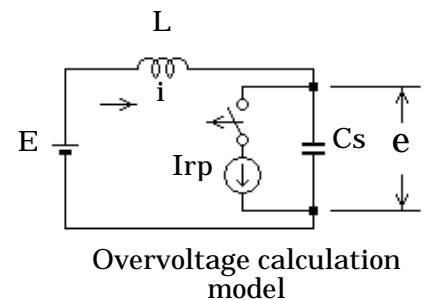where C_j is junction capacity and C_s' is the floating capacity of wiring.



Overvoltage calculation model

At this time, I_{rp} reaches the maximum reverse recovery current. Let $t_4 - t_3 = 0$, and the following holds:

$$E = L \frac{d^2 q}{dt^2} + \frac{q}{Cs} \text{ -----(4)}$$

$$q = CsE + A \cos \frac{t}{\sqrt{LCs}} + B \sin \frac{t}{\sqrt{LCs}} \text{ -----(5)}$$

$$e = E + \frac{A}{Cs} \cos \frac{t}{\sqrt{LCs}} + \frac{B}{Cs} \sin \frac{t}{\sqrt{LCs}} \text{ -----(6)}$$

$$i = \frac{dq}{dt} = -\frac{A}{\sqrt{LCs}} \sin \frac{t}{\sqrt{LCs}} + \frac{B}{\sqrt{LCs}} \cos \frac{t}{\sqrt{LCs}} \text{ -----(7)}$$

Under the initial conditions, and when $t = 0$,

$$e = E \quad i = I_{rp}$$

Therefore,

from Equation (6), $A = 0$. From Equation (7), $B = I_{rp} \sqrt{LCs}$ holds.

Therefore, $e = E + I_{rp} \sqrt{\frac{L}{Cs}} \sin \frac{t}{\sqrt{LCs}} \text{ -----(8)}$

This means that the diode's maximum reverse voltage e becomes

$$e = E + I_{rp} \sqrt{\frac{L}{Cs}} \text{ -----(9)}$$

Since Cs is small (several pico-Farads to dozens of pico-Farads), surge voltage occurs when wiring inductance L is large.

Suppressing commutation surge voltage

- 1) Add capacitor C in parallel with the diode to absorb surge voltage. This capacitor C is called C between A and K .
- 2) Use an avalanche diode to absorb surge reverse power.

*** Information about a new product ***

Surface-mount surge suppressor diode: DAM1MA68/75/82 (1W class)

DAM3MA68/75/82 (3W class)

Major applications: Protection of electronics in automotive products and general industrial equipment