

## Hitachi Power Devices Technical Information PD Room

This issue presents snubber circuits, which are almost always required in power switching devices.

**The snubber circuit** is a circuit inserted to protect a switching device from overvoltage due to accumulated energy in the wiring inductance of the circuit when the switching device is turned off. Snubber circuits generally come in two types: a non-polarized type consisting of capacitors ( $C_s$ ) and resistors ( $R_s$ ) and a polarized type with  $C_s$  and  $R_s$  plus a diode. IGBT uses a polarized type, which effectively suppresses surge voltage. (The snubber circuit is also described in the IGBT Total Module Catalog No. EC-E704P. If necessary, please refer to this material.)

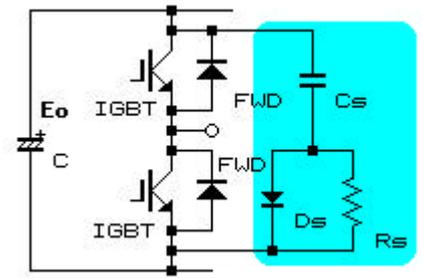


Fig.1 P-N Snubber Circuit

### 1) Snubber circuit operation

A typical P-N snubber circuit is described above Fig. 1.

Fig. 2 represents a circuit in the overvoltage occurrence mode of a bottom-arm IGBT at the time of turning off. Fig. 3 represents an equivalent circuit in a transient state at the same time.

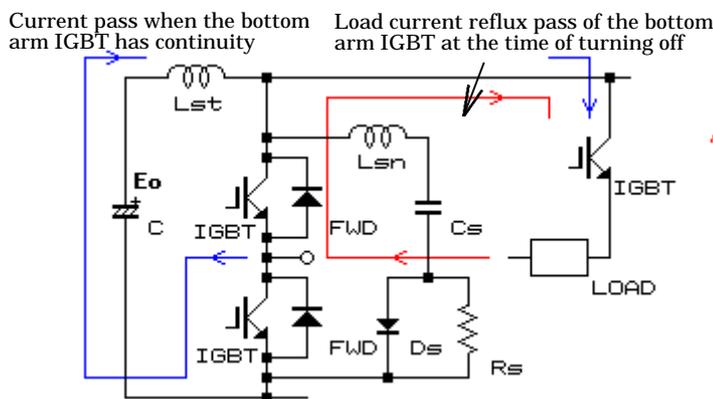


Fig.2 Turn-off mode of bottom arm IGBT

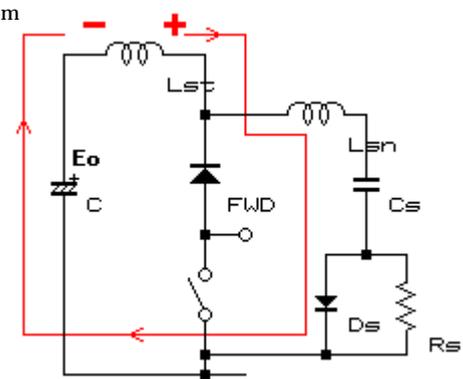


Fig. 3 Equivalent circuit when the circuit indicated in the left-hand figure is in a transient state

Fig. 2 represents changes in the current pass when the bottom IGBT, which was on, is turned off. When the bottom arm IGBT is turned off, the load current passes through the FWD at the top arm and is refluxed. Discharge of energy accumulated in the  $L_{st}$  is applied to the bottom arm IGBT as an overvoltage because the absence of a snubber circuit results in the loss of a discharge destination. Installing a snubber circuit results in  $L_{st}$  energy passing through the snubber circuit and being refluxed, as shown in Fig. 3. This allows overvoltage suppression. However, in reality, the snubber circuit also has wiring inductance  $L_{sn}$ , which may cause overvoltage.

**How can  $L_{st}$  and  $L_{sn}$  be reduced? The key is to choose the right components and lay them out appropriately.**

2) Current and voltage waveforms when a snubber circuit is involved

Let us consider current and voltage waveforms in the circuit indicated in Fig. 2, when the IGBT is turned off.

Fig. 4 represents current and voltage waveforms of the IGBT device when turned off. Use of a snubber circuit inhibits surge voltage stemming from wiring inductance  $L_{st}$  to  $E_o + \Delta V_f$ .

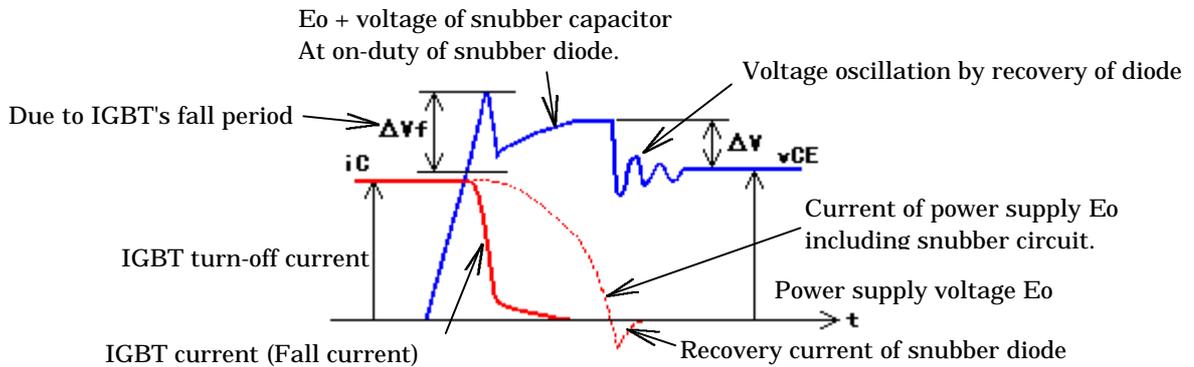


Fig.4 IGBT current  $i_C$  & voltage  $v_{CE}$  at snubber circuit operation.

Fig. 5 represents current and voltage waveforms of the snubber diode  $D_s$  when the snubber circuit functions. The items can be determined with the following equations:

$$TS = \frac{2\rho\sqrt{Lst \times Cs}}{4} \text{ -----Equation (1)}$$

$$\Delta V = Ic \times \sqrt{\frac{Lst}{Cs}} \text{ -----Equation (2)}$$

$I_c$  is an IGBT turn-off current

$$DVf = Lsn' dic/dt + Vfr \text{ ---Equation (3)}$$

where  $L_{sn}$  is the snubber circuit inductance as viewed from IGBT's collector and emitter terminals, and  $V_{fr}$  is about 50 V. The  $dic/dt$  is the current change ratio in IGBT's fall period.

$$TN = 3 \times Cs \times Rs \text{ -----Equation (4)}$$

where  $T_N$  is a time required to discharge 95% of the overcharge voltage of the  $C_s$ .  $R_s$  must be set to such a value that makes  $T_s + T_n < 1/f_c$ .

In the above equation, in the case of a three-phase circuit, the  $T_s$  in Equation (1) becomes  $\sqrt{3}$  times, and the  $\Delta V$  in Equation (2) becomes  $1/\sqrt{3}$ .

Because of space limitations, the constants for each IGBT current class will be described in the next issue.

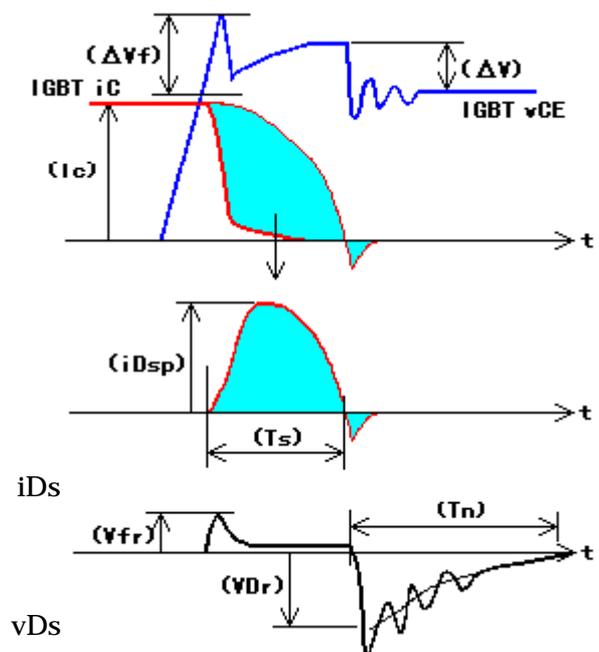


Fig.5 Each portion of snubber circuit.

Next issue : 1) Snubber circuit constants of IGBT  
2) How surge voltage occurs of diode